

Experiment No 5:
Combinational Circuits:
Structural Modeling Simulation

Submitted To:

Ubaid Ullah Fayyaz

Submitted By:

Muhammad Aqib Wazir

2022-EE-172

Section D

Digital System

**University Of Engineering and
Technology, Lahore**

Truth table

characters	A1	A0	B1	B0	seg a	seg b	seg c	seg d	seg e	seg f	seg g
0	0	0	0	0	0	0	0	0	0	0	1
1	0	0	0	1	1	0	0	1	1	1	1
2	0	0	1	0	0	0	1	0	0	1	0
3	0	0	1	1	0	0	0	0	1	1	0
4	0	1	0	0	1	0	0	1	1	0	0
5	0	1	0	1	0	1	0	0	1	0	0
6	0	1	1	0	0	1	0	0	0	0	0
7	0	1	1	1	0	0	0	1	1	1	1
8	1	0	0	0	0	0	0	0	0	0	0
9	1	0	0	1	0	0	0	0	1	0	0
A	1	0	1	0	0	0	0	1	0	0	0
B	1	0	1	1	1	1	0	0	0	0	0
C	1	1	0	0	0	1	1	0	0	0	1
D	1	1	0	1	1	0	0	0	0	1	0
E	1	1	1	0	0	1	1	0	0	0	0
F	1	1	1	1	0	1	1	1	0	0	0

[illegible]

K-maps

Seg A:

AB \ CD	00	01	11	10
00	0	1	0	0
01	1	0	0	0
11	0	1		0
10	0	0	1	0

$$(\bar{A}+D) \cdot (A+\bar{C}) \cdot (\bar{B}+\bar{C}) \cdot (B+D) \cdot (A+B+C) \cdot (A+\bar{B}+\bar{D})$$

Seg B:

AB \ CD	00	01	11	10
00	0	0	0	0
01	0	1	0	1
11	1	0	1	1
10	0	0	1	0

$$(B+C) \cdot (B+D) \cdot (A+\bar{C}+\bar{D}) \cdot (A+C+D) \cdot (\bar{A}+C+\bar{D})$$

Seg C:

AB \ CD	00	01	11	10
00	0	0	0	1
01	0	0	0	0
11	1	0	1	1
10	0	0	0	0

$$(A+C) \cdot (A+\bar{D}) \cdot (A+\bar{B}) \cdot (C+\bar{D}) \cdot (\bar{A}+B)$$

Seg D

AB \ CD	00	01	11	10
00	0	1	0	0
01	1	0	1	0
11	0	0	1	0
10	0	0	0	1

$$(\bar{A}+C) \cdot (\bar{B}+C+D) \cdot (A+B+D) \cdot (B+\bar{C}+D) \cdot (\bar{B}+\bar{C}+D)$$

Seg E

AB \ CD	00	01	11	10
00	0	1	1	0
01	1	1	1	0
11	0	0	0	0
10	0	1	0	0

$$(B+D) \cdot (\bar{A}+\bar{C}) \cdot (\bar{A}+\bar{B}) \cdot (\bar{C}+D)$$

Seg F

AB \ CD	00	01	11	10
00	0	1	1	1
01	0	0	1	0
11	0	1	0	0
10	0	0	0	0


$$(\bar{A}+\bar{C}) \cdot (\bar{B}+D) \cdot (C+D) \cdot (A+\bar{B}+C) \cdot (\bar{A}+B)$$

Seg G

AB \ CD	00	01	11	10
00	1	1	0	0
01	0	0	1	0
11	1	0	0	0
10	0	0	0	0

$$(\bar{A}+B) \cdot (\bar{C}+D) \cdot (\bar{A}+D) \cdot (B+\bar{C}) \cdot (A+\bar{B}+C)$$

Circuit diagram using vivado:

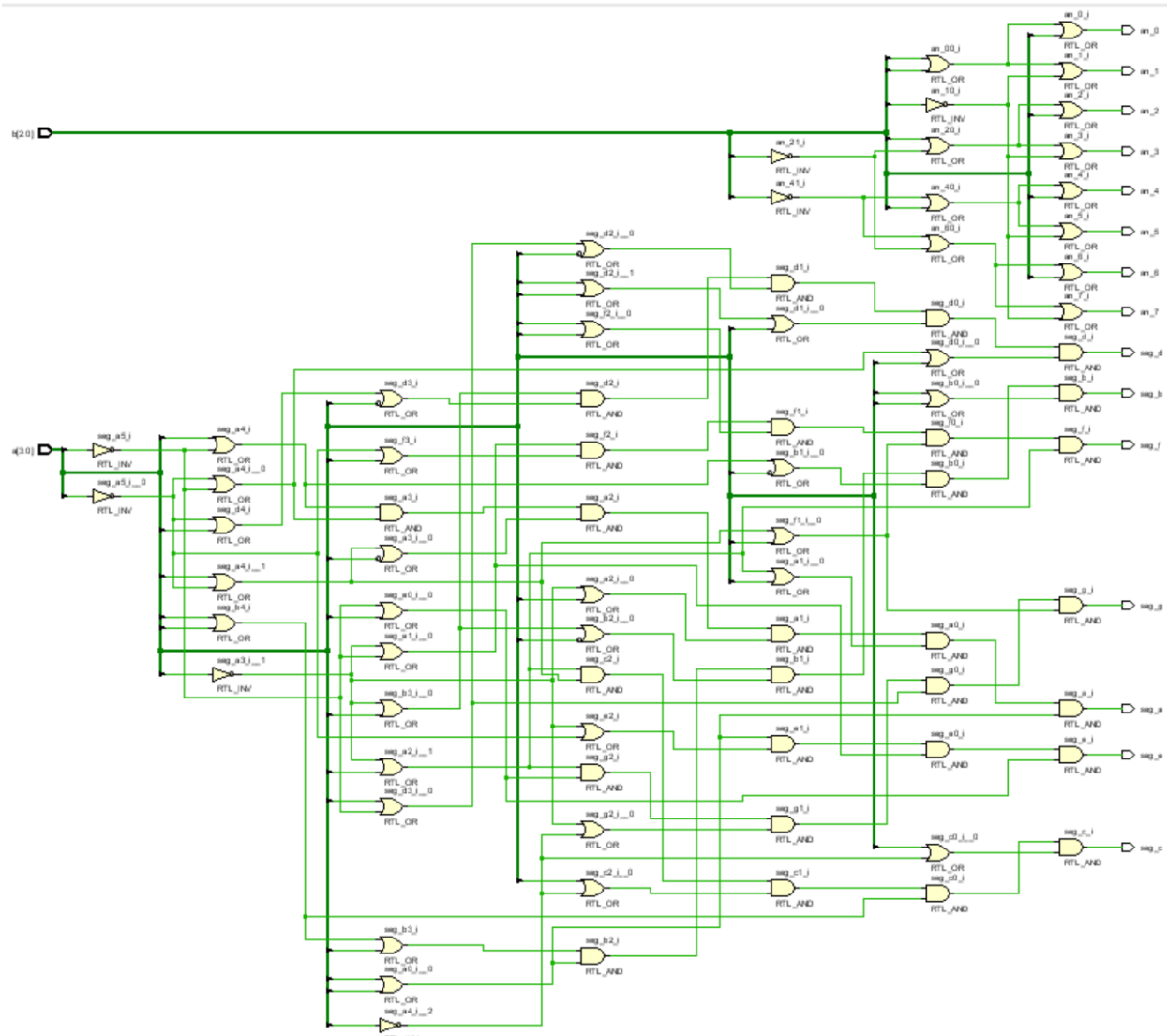

Maximum combinational delay in Synthesis:

Name	Slack ^1	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock	Destination Clock	Exception
↳ Path 1	∞	3	2	8	b[0]	an_2	6.836	5.230	1.606	∞	input port clock		
↳ Path 2	∞	3	2	8	b[2]	an_3	6.805	5.199	1.606	∞	input port clock		
↳ Path 3	∞	3	2	8	b[2]	an_7	6.804	5.199	1.606	∞	input port clock		
↳ Path 4	∞	3	2	7	a[1]	seg_f	6.798	5.192	1.606	∞	input port clock		
↳ Path 5	∞	3	2	7	a[1]	seg_b	6.792	5.187	1.606	∞	input port clock		
↳ Path 6	∞	3	2	7	a[1]	seg_a	6.792	5.186	1.606	∞	input port clock		
↳ Path 7	∞	3	2	8	b[0]	an_5	6.789	5.184	1.606	∞	input port clock		
↳ Path 8	∞	3	2	8	b[0]	an_4	6.788	5.182	1.606	∞	input port clock		
↳ Path 9	∞	3	2	7	a[3]	seg_d	6.784	5.178	1.606	∞	input port clock		
↳ Path 10	∞	3	2	8	b[0]	an_6	6.779	5.173	1.606	∞	input port clock		

Maximum combinational delay in Implementation:

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock	Destination Clock	Exception
↳ Path 1	∞	3	2	8	b[1]	an_6	11.080	5.339	5.741	∞	input port clock		
↳ Path 2	∞	3	2	7	a[2]	seg_a	10.407	5.414	4.993	∞	input port clock		
↳ Path 3	∞	3	2	7	a[2]	seg_b	10.150	5.159	4.991	∞	input port clock		
↳ Path 4	∞	3	2	8	b[1]	an_7	10.114	5.400	4.714	∞	input port clock		
↳ Path 5	∞	3	2	8	b[1]	an_2	10.110	5.192	4.917	∞	input port clock		
↳ Path 6	∞	3	2	8	b[1]	an_3	9.927	5.406	4.521	∞	input port clock		
↳ Path 7	∞	3	2	7	a[2]	seg_f	9.832	5.397	4.434	∞	input port clock		
↳ Path 8	∞	3	2	8	b[1]	an_0	9.649	5.382	4.268	∞	input port clock		
↳ Path 9	∞	3	2	7	a[3]	seg_d	9.623	5.382	4.241	∞	input port clock		
↳ Path 10	∞	3	2	7	a[2]	seg_e	9.298	5.137	4.161	∞	input port clock		

Resource Utilization Summary:

1. Slice Logic

Site Type	Used	Fixed	Available	Util%
Slice LUTs*	8	0	63400	0.01
LUT as Logic	8	0	63400	0.01
LUT as Memory	0	0	19000	0.00
Slice Registers	0	0	126800	0.00
Register as Flip Flop	0	0	126800	0.00
Register as Latch	0	0	126800	0.00
F7 Muxes	0	0	31700	0.00
F8 Muxes	0	0	15850	0.00

4. IO and GT Specific

Site Type	Used	Fixed	Available	Util%
Bonded IOB	22	0	210	10.48
Bonded IPADs	0	0	2	0.00
PHY_CONTROL	0	0	6	0.00
PHASER_REF	0	0	6	0.00
OUT_FIFO	0	0	24	0.00
IN_FIFO	0	0	24	0.00
IDELAYCTRL	0	0	6	0.00
IBUFDS	0	0	202	0.00
PHASER_OUT/PHASER_OUT_PHY	0	0	24	0.00
PHASER_IN/PHASER_IN_PHY	0	0	24	0.00
IDELAYE2/IDELAYE2_FINEDELAY	0	0	300	0.00
ILOGIC	0	0	210	0.00
OLOGIC	0	0	210	0.00

7. Primitives

Ref Name	Used	Functional Category
OBUF	15	IO
LUT3	8	LUT
LUT4	7	LUT
IBUF	7	IO